


AI On Chip 2022

Assignment 4

MAC Implementation & Analyzation



PE(**P**rocessing **E**lement)

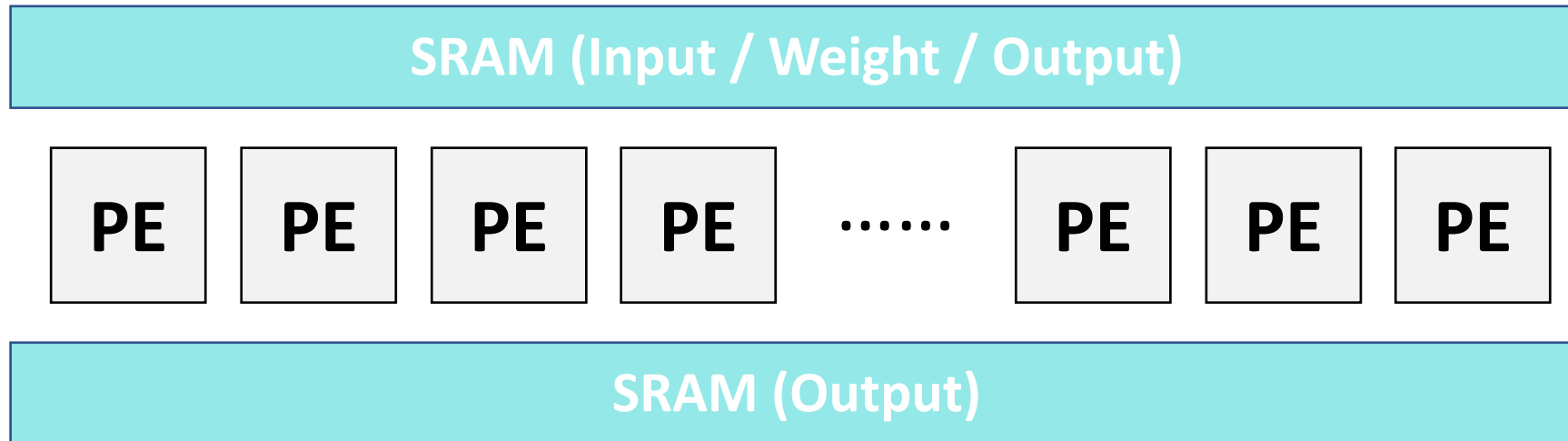- It's the computation unit in AI Accelerator
- There are a lot of PEs in AI Accelerator
- PE loads data from SRAM, compute and save the result back to SRAM
- **SRAM can be divided into 3 types** according to the data it stores
 - Input feature map
 - Weight
 - Output feature map





PE(Processing Element)

  - It's the computation unit in AI Accelerator
- There are a lot of PEs in AI Accelerator
- Take 3*3, 1 stride Convolution for example





PE(Processing Element)

  - It's the computation unit in AI Accelerator
- There are a lot of PEs in AI Accelerator
- Take 3*3, 1 stride Convolution for example





PE(Processing Element)

  - It's the computation unit in AI Accelerator
- There are a lot of PEs in AI Accelerator
- Take 3*3, 1 stride Convolution for example




PE(Processing Element)

  - It's the computation unit in AI Accelerator
- There are a lot of PEs in AI Accelerator
- Take 3*3, 1 stride Convolution for example




PE(Processing Element)

 - How about 5*5 convolution in these 3*3 PEs ?




4 PEs each convolution

 This method will waste
a lot of computation opportunities




PE(Processing Element)


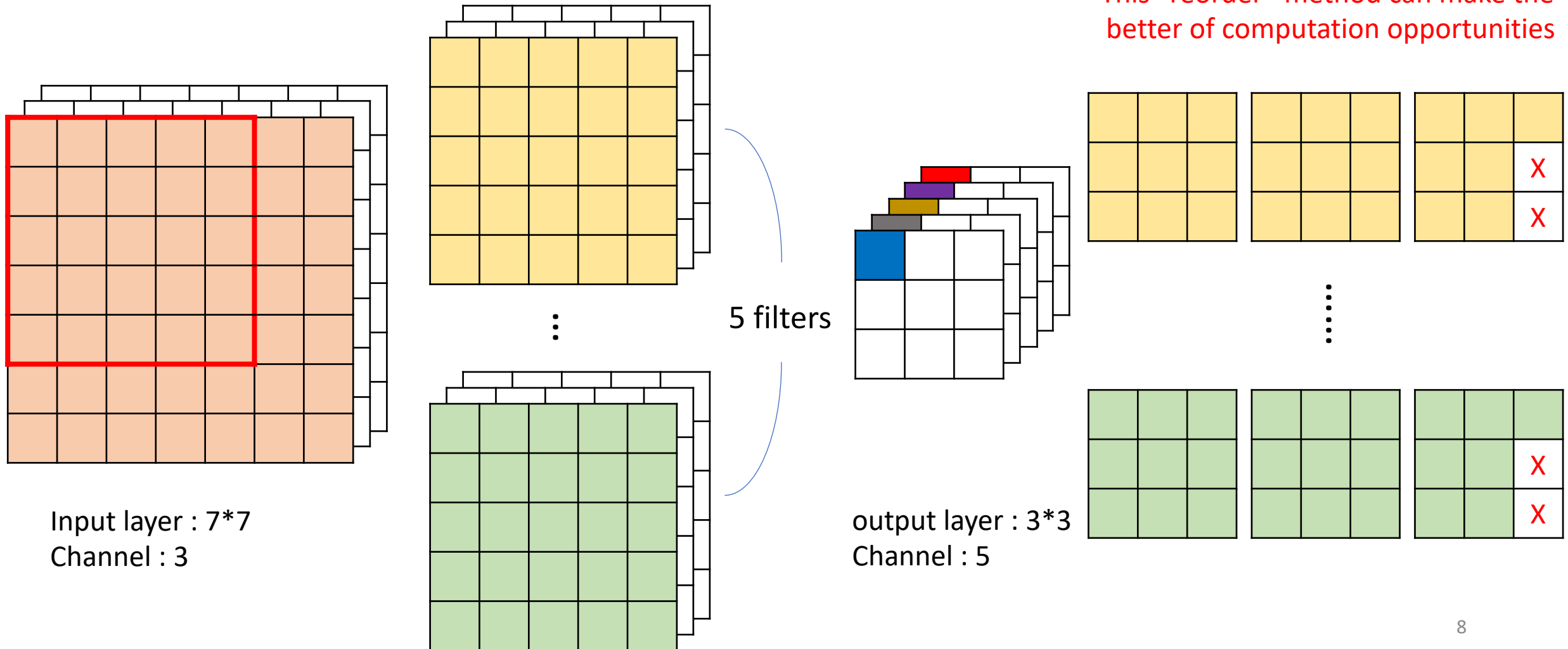
- How about 5*5 convolution in these 3*3 PEs ?



PE(Processing Element)

- We can view 3*3 PE as 9 MAC operations
- MAC (Multiply Accumulate)

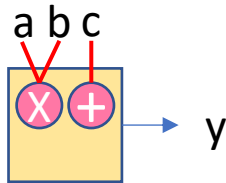
$$y \leftarrow a * b + c$$

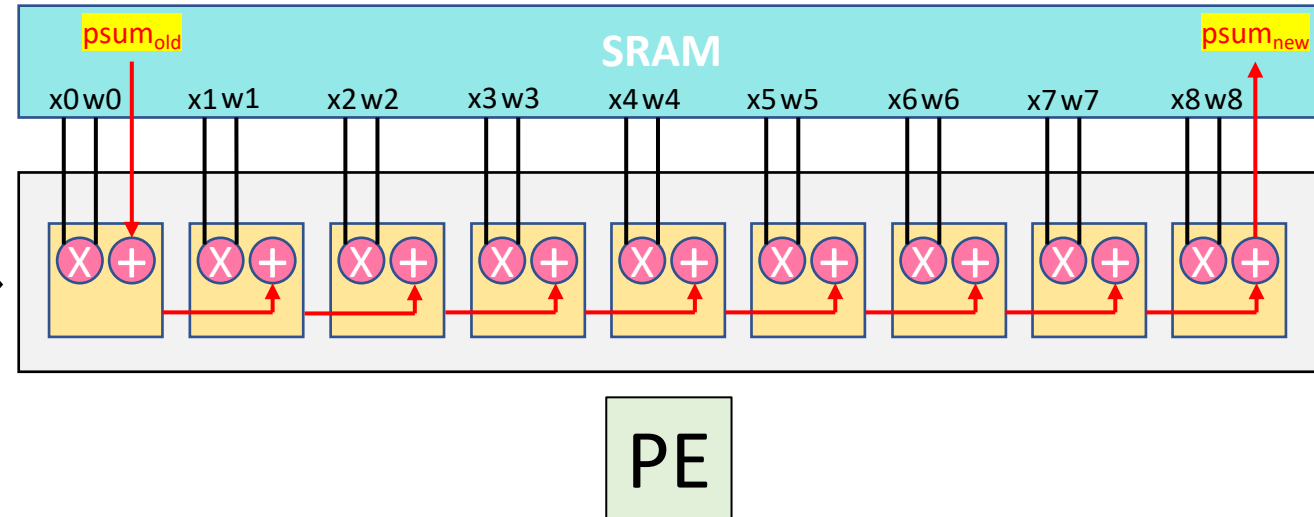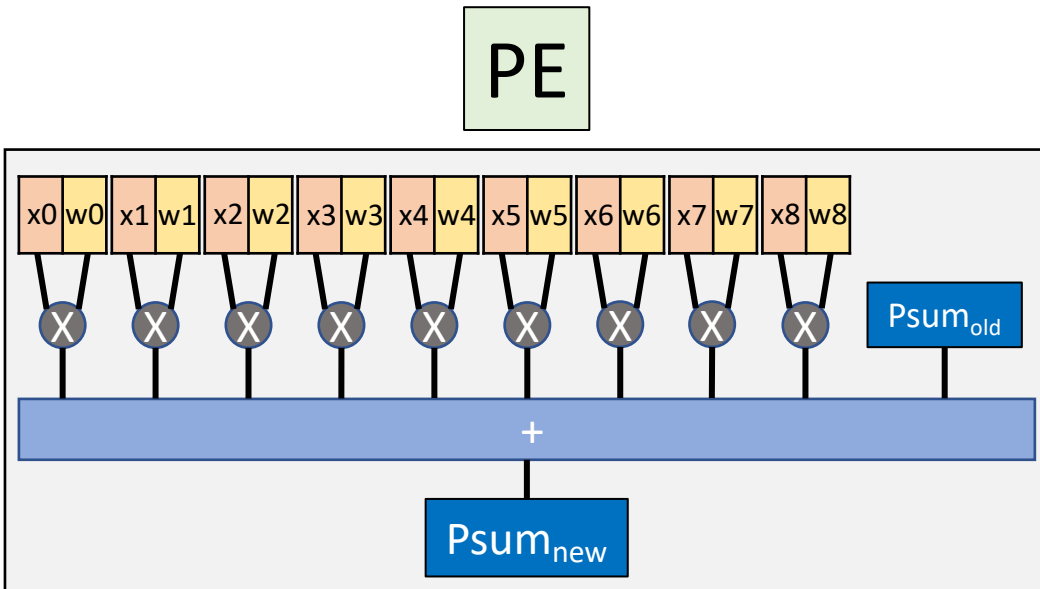


```
psummid ← x0 * w0 + psumold
psummid ← x1 * w1 + psummid
psummid ← x2 * w2 + psummid
psummid ← x3 * w3 + psummid
psummid ← x4 * w4 + psummid
psummid ← x5 * w5 + psummid
psummid ← x6 * w6 + psummid
psummid ← x7 * w7 + psummid
psumnew ← x8 * w8 + psummid
```

MAC (Multiply Accumulate)
 
$$y \text{ (12bits)} \leftarrow a \text{ (4bits)} \times b \text{ (4bits)} + c \text{ (12bits)}$$





Just ignore it, if it overflow, it will become noise.

MAC (**M**ultiply **A**ccumulate)

If you don't know what is CSA / CPA
Please see the next page first

Multiply (3 steps)

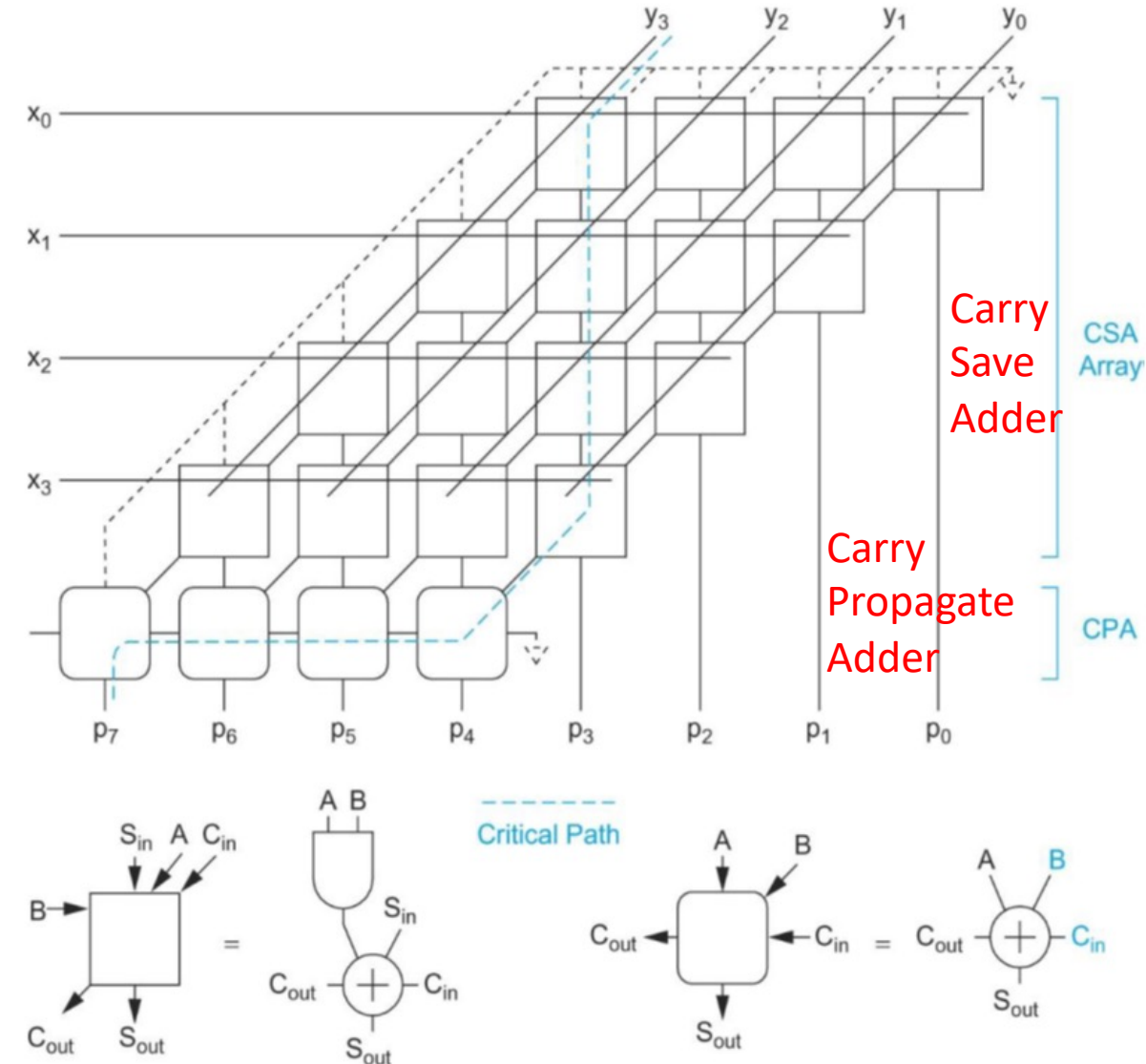 1. **P**artial **P**roduct **G**enerator (PPG)
 - Do AND operation on each bit of x & y
 - Produce the pink points
2. **P**artial **P**roduct **R**eduction **T**ree (PPRT)
 - Efficiently add all pink points, we use CSA
3. **C**arry-**P**ropagate **A**dder (CPA)
 - Last Adder



CPA vs CSA

Take 3 numbers addition as example


$$\begin{array}{r} x_3 x_2 x_1 x_0 \\ +) y_3 y_2 y_1 y_0 \\ +) z_3 z_2 z_1 z_0 \end{array}$$

M = How many numbers to add = 3
N = How many bits in a number = 4

Carry-Propagate Adder (delay : (M-1) * N FAs)


Step 1 : $\text{Sum}_{x+y} = x + y$

Time : N FAs

 

Step 2 : $\text{Sum} = \text{Sum}_{x+y} + z$


Time : N FAs

 

Carry-Save Adder (delay : (M-2) + N FAs)


Step 1 : Each bit does FA independently

Time : 1 FAs

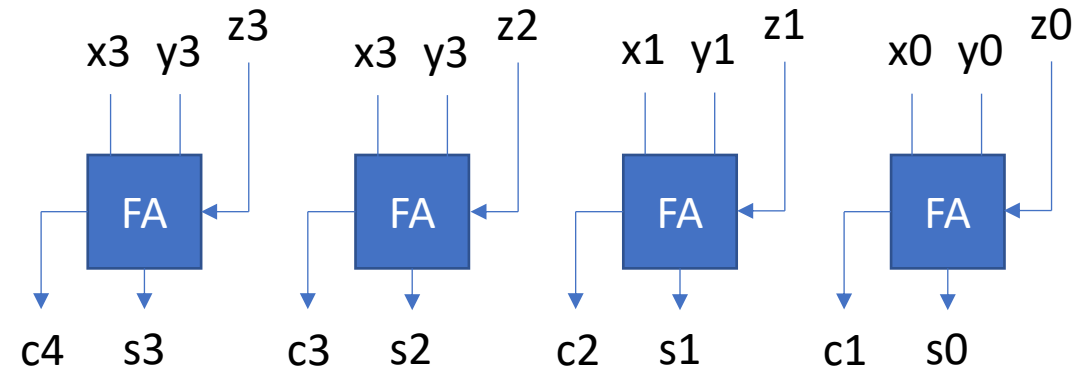



Step 2 : Do Carry-Propagate, $\text{Sum} = c + s$

Time : N FAs

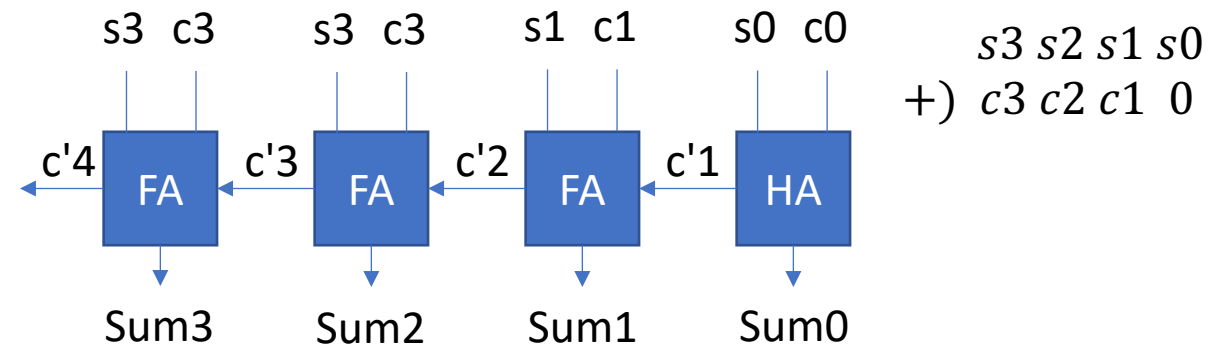


Supplement : Another PPRT Method, **Wallace Tree**

Take 8*8 multiply as example

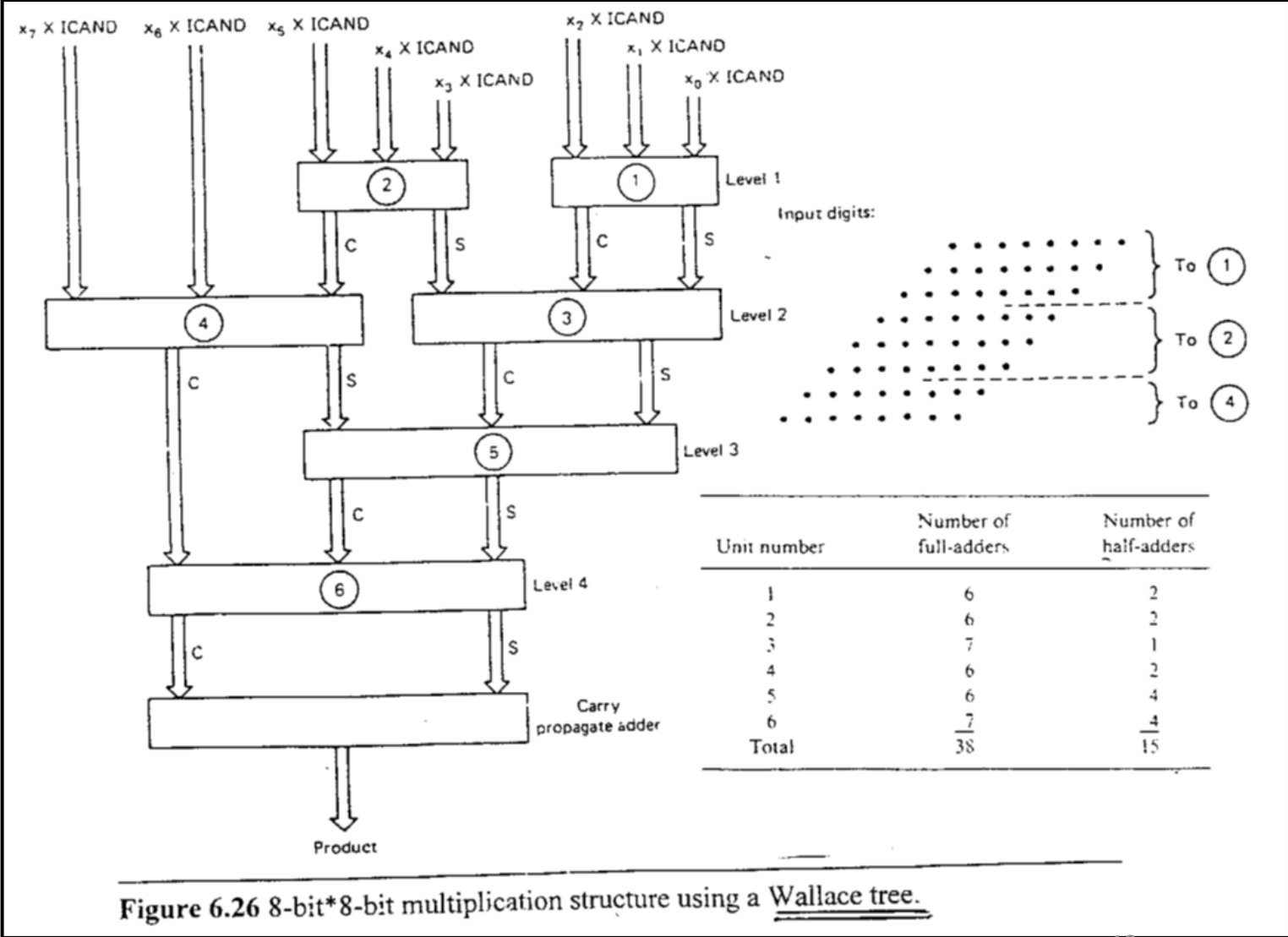 

Homework (Verilog & Report)

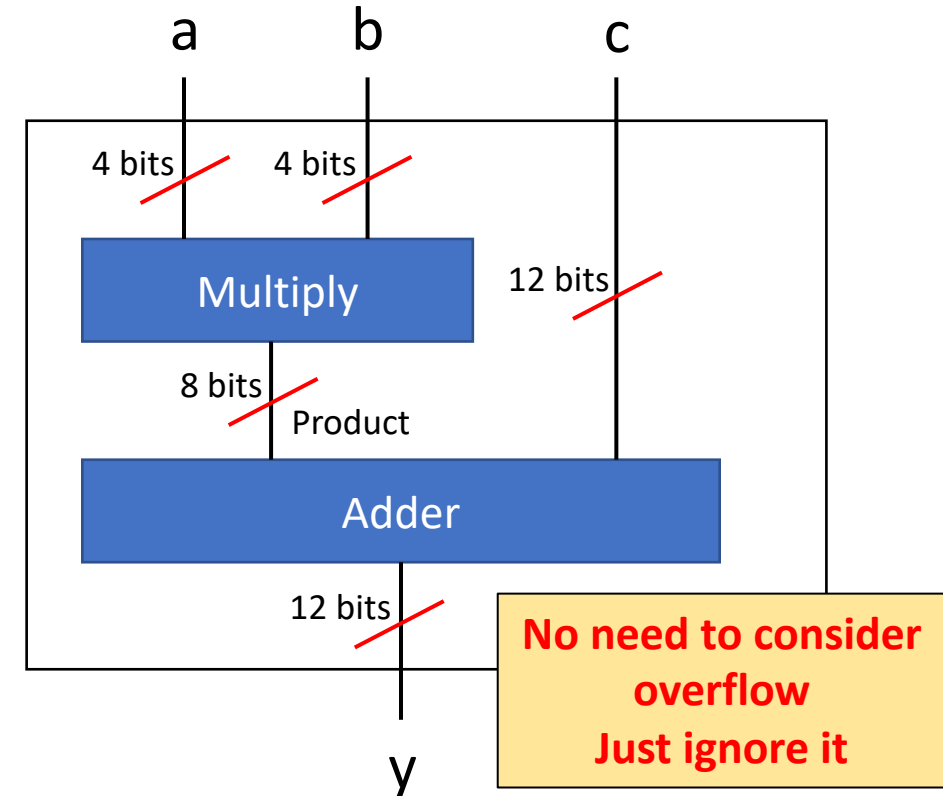1. Implement Half-adder & Full-adder
2. Implement a 4-bit MAC mentioned in this ppt
 - You can only use the components below
 - Half-Adder / Full-Adder you implemented
 - Verilog Built-in AND gate
 - Pass all test data
 - Analyze how many Half Adder and Full Adder you use
 - Analyze the delay / latency of your 4-bit MAC



3. Use 4-bit MAC to combine a 8-bit MAC
 - Pass all test data
 - Explain what's the difference between
 - ① A primitive 8-bit MAC (same method as 4-bit MAC you implemented, but $(a, b, c) = (8, 8, 24)$ bits)
 - ② The combined 8-bit MAC (combined by 4-bit MAC)
4. Use primitive 8-bit MAC to explain the difference before and after using Wallace Tree
 - Please explain what is Wallace Tree first
 - Just think and explain, do not need to implement

Homework – Verilog Component Format

1. HalfAdder

- File name : HA.v
- Module name : HA

2. FullAdder

- File name : FA.v
- Module name : FA

3. 4-bit MAC

- File name : MAC_4bit.v
- Module name : MAC_4bit

4. 8-bit MAC

- File name : MAC_8bit.v
- Module name : MAC_8bit

4-bit MAC

```
`include "HA.v"
`include "FA.v"
module MAC_4bit (
    input [3:0] a,
    input [3:0] b,
    input [11:0] c,
    output [11:0] result,
    output cout
);

/* Here is your code */

endmodule
```

8-bit MAC

```
`include "MAC_4bit.v"
module MAC_8bit (
    input [7:0] a,
    input [7:0] b,
    input [23:0] c,
    output [23:0] result,
    output cout
);

/* Here is your code */

endmodule
```

Homework – Report Format

Please turn the report into PDF

1. 4-bit MAC

- Screenshot all pass screen
- The analyzation of your 4-bit MAC
 - Simply introduce your 4-bit MAC
 - (Hardware Resource) Count how many HA & FA you used
 - (Time Delay) Count the delay / latency of your 4-bit MAC (you can use FA as time unit)

2. 8-bit MAC

- Screenshot all pass screen
- Detailly introduce how you combined it through 4-bit MAC you implemented
- Explain what's the difference (hardware resource / delay) between
 - ① A primitive 8-bit MAC (same method as 4-bit MAC you implemented, but $(a, b, c) = (8, 8, 24)$ bits)
 - ② The combined 8-bit MAC (combined by 4-bit MAC you implemented)

3. Wallace Tree

- Introduce what is Wallace Tree
- Explain the difference before and after using Wallace Tree with the primitive 8-bit MAC

Homework – File Structure

